

DESIGN SHOWCASE


Three ICs Produce Pure Sine Waves

A TTL counter, an 8-channel analog multiplexer, and a fourth-order lowpass filter can generate 1- to 25-kHz sine waves with a THD better than -80dB (Figure 1). The circuit cascades the two second-order, continuous-time Sallen-Key filters within IC₃ to implement the fourth-order lowpass filter. Two resistive dividers connected from ground to V_{DD} and ground to V_{SS} provide bipolar dc inputs to the multiplexer.

To operate the circuit, you must first choose the filter's cutoff frequency, f_c , by tying IC₃'s D₀ through D₆ inputs to 5V or ground. The cutoff frequency can be at 128 possible levels between 1 and 25kHz depending on those seven digital input levels. Because Figure 1 ties D₀ through D₆ to ground, f_c equals 1kHz. The 100k Ω potentiometer adjusts the output level between V_{DD} -1.5V and V_{SS} +1.5V.

The clock's input frequency must be eight times higher than the filter's f_c . The multiplexer then produces an eight-times oversampled staircase approximation of a sine wave. Eight-times oversampling greatly simplifies the smoothing requirements of the lowpass filter by pushing the first significant harmonic out to seven times the fundamental. All higher-order harmonics are removed by IC₃, which includes an uncommitted amplifier for setting the output level.

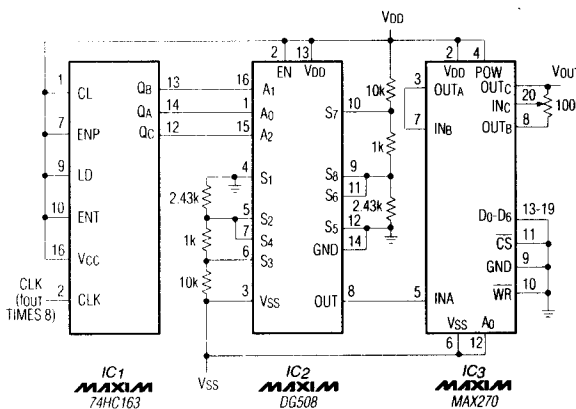The frequency domain offers a view of the filter's operation. Smaller harmonics in the multiplexer's output spectrum (Figure 2a), caused by inaccuracies in the voltage dividers, are insignificant with respect to the larger-amplitude harmonics associated with the staircase approximation. In the filtered output (Figure 2b), all harmonics are lost in the noise floor of the spectrum analyzer.



NOTES:
V_{DD} TYPICALLY IS 5V
V_{SS} TYPICALLY IS -5V

Figure 1. This circuit produces a pure, -80dB THD sine wave whose frequency equals f_c of the IC₃ filter.

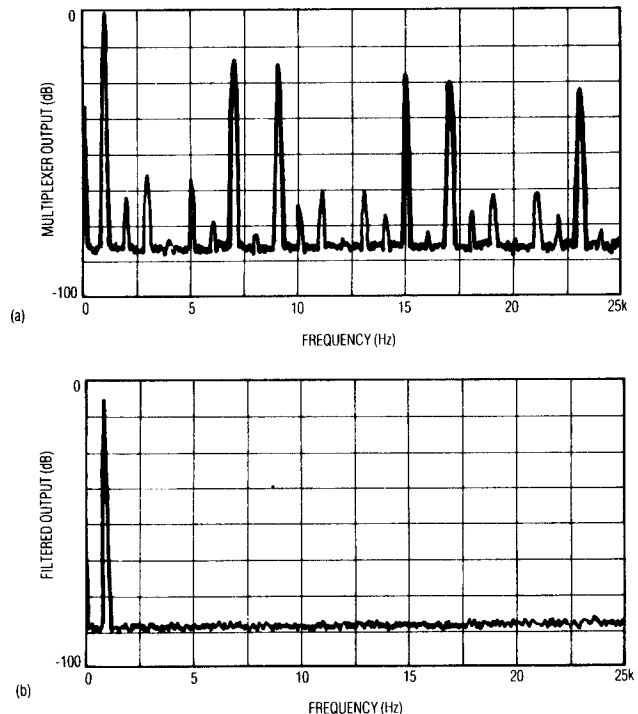


Figure 2. The circuit's approximation process generates large harmonics in the multiplexer's output spectrum (a), which the filter attenuates to a level below the spectrum analyzer's noise floor (b).

(Circle 7)