

DESIGN SHOWCASE

Regulated Step-Up Converter Provides High Efficiency Without Inductors

Two 8-pin ICs (**Figure 1**) form a regulator circuit that converts the 3V output of a lithium battery to 5V, and delivers load currents as high as 100mA. The circuit operates without inductors or transformers, and draws only 200 μ A of quiescent current. It offers 81% efficiency with a 100mA load and 84% with a 20mA load, at $V_{IN} = 3V$. The efficiency rises as V_{IN} falls. At $V_{IN} = 2.7V$, for example — the lithium cell's loaded output for most of its operating life — the efficiency for a 40mA load current is 90%.

Voltage from the lithium battery (a $\frac{2}{3}$ -A size Duracell DL123A) is doubled by the high-current charge pump IC₁. The Schottky diode (D₁) is included to assure startup in this configuration, and has no effect on efficiency because it doesn't conduct load current during normal operation.

IC₂ is a linear regulator whose dropout voltage is only 40mV at $I_{LOAD} = 40mA$. This load, allowed to drain the battery until $V_{OUT} = 4.5V$, yields a 16-hour battery life. Reducing the load to 20mA extends battery life to 36 hours.

(Circle 2)

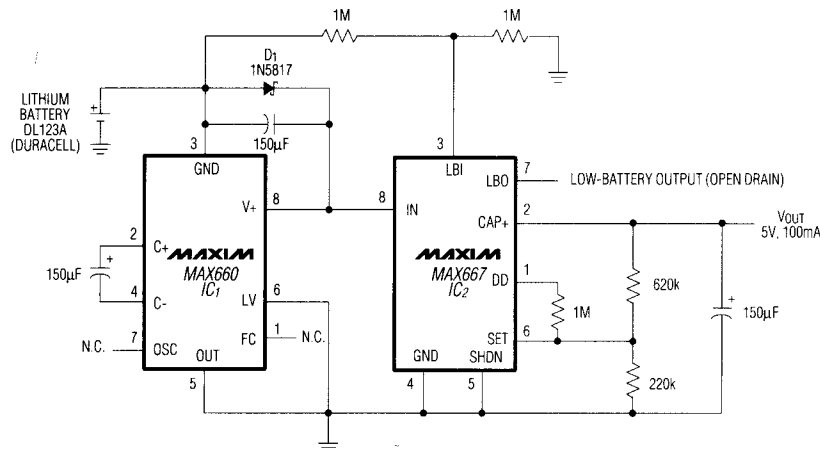


Figure 1. Operating without magnetic components, this circuit derives a regulated 5V from a 3V lithium battery and delivers load currents as high as 100mA.