

An adjustable power supply should provide a range that includes 0V. However, as shown in Figure 1, a typical adjustable regulator does not facilitate adjustment to voltages lower than V_{REF} (the internal bandgap voltage). Feedback-loop summing junction ADJ must be biased at V_{REF} to provide linear operation. The lowest output voltage available from this circuit is provided when $R1 = 0\Omega$. For the MIC29152 LDO Regulator $V_{REF} = 1.24V$. $V_{OUT} = V_{REF}(1+R1/R2)$.

The circuit of Figure 2 provides adjustability down to 0V by controlling the ground reference of the feedback divider. Moreover, it makes use of the internal bandgap reference to provide both accuracy and economy. Non-inverting amplifier A2 senses V_{REF} (via V_{ADJ}) and provides a gain of just slightly more than unity. When $R5$ is adjusted to supply ground to voltage follower A1 then ground is also applied to the bottom of feedback voltage divider $R1$ and $R2$, and operation is

identical to the circuit of Figure 1 (adjusted to provide maximum output voltage). Conversely, when $R5$ is adjusted so the input to voltage follower A1 is taken directly from the output of amplifier A2 the bottom of voltage divider $R1$ and $R2$ is biased such that V_{ADJ} will equal V_{REF} when V_{OUT} is 0V. Rotation of $R5$ results in a smooth variation of output voltage from 0V to the upper design value, determined by $R1$ and $R2$, again: $V_{OUT(max)} = V_{REF}(1+R1/R2)$.

The gain of amplifier A2 is $1+R4/R3 = 1.05$, in this example. It is interesting to note that the portion of gain above unity is the reciprocal of the attenuation ratio afforded by feedback divider $R1$ and $R2$; i.e., $R4/R3 = 1/(R1/R2)$. To provide optimal ratio matching, resistors $R3$ and $R4$ have been chosen to be the same values and types as their counterparts $R1$ and $R2$, respectively.

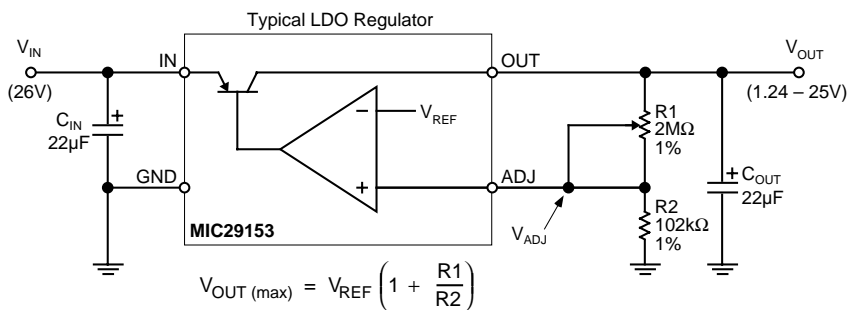


Figure 1. Typical Adjustable Regulator

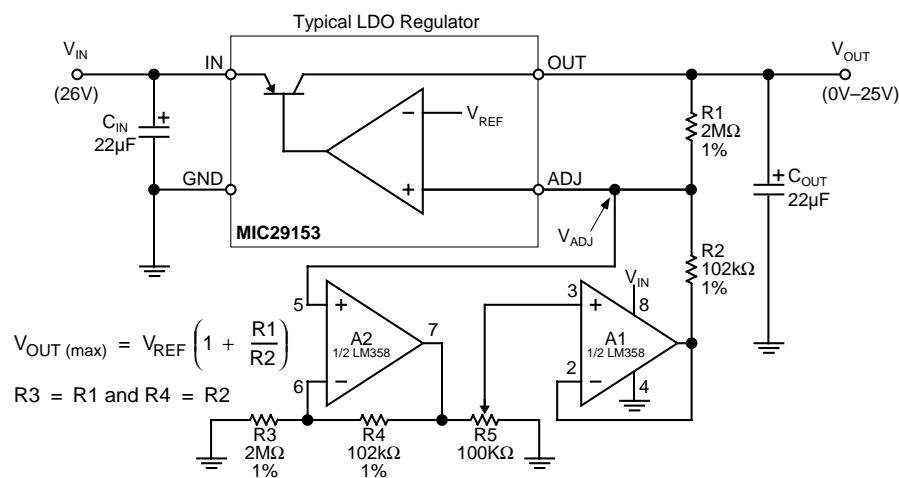


Figure 2. 0V-25V Adjustable Regulator