# **SanDisk Application Note**

# UniDirectional to BiDirectional Serial Data Conversion for the MultiMediaCard



SanDisk Corporation 140 Caspian Court Sunnyvale, CA 94089 TEL: 408-542-0500 FAX: 408-542-0503 URL: http://www.sandisk.com

SanDisk<sup>®</sup> Corporation general policy does not recommend the use of its products in life support applications where in a failure or malfunction of the product may directly threaten life or injury. Per SanDisk Terms and Conditions of Sale, the user of SanDisk products in life support applications assumes all risk of such use and indemnifies SanDisk against all damages.

The information in this document is subject to change without notice.

SanDisk Corporation shall not be liable for technical or editorial errors or omissions contained herein; nor for incidental or consequential damages resulting from the furnishing, performance, or use of this material.

All parts of SanDisk documentation are protected by copyright law and all rights are reserved. This documentation may not, in whole or in part, be copied, photocopied, reproduced, translated, or reduced to any electronic medium or machine readable form without prior consent, in writing, from SanDisk Corporation.

SanDisk and the SanDisk logo are registered trademarks of SanDisk Corporation.

Product names mentioned herein are for identification purposes only and may be trademarks and/or registered trademarks of their respective companies.

© 1999 SanDisk Corporation. All rights reserved.

SanDisk products are covered or licensed under one or more of the following U.S. Patent Nos. 5,070,032; 5,095,344; 5,168,465; 5,172,338; 5,198,380; 5,200,959; 5,268,318; 5,268,870; 5,272,669; 5,418,752; 5,602,987. Other U.S. and foreign patents awarded and pending.

Lit. No. 80-13-00136 Rev. 1 6/99

Printed in U.S.A.

# **Considerations for Interfacing to SanDisk Flash**

Introduction

Althought SanDisk's MultiMediaCard already has a Serial Peripheral Interface (SPI), data throughput and faster transfers can be achieved when the card is in the MultiMediaCard mode. The design described in this application note provides a simple means to translate an existing SPI or serial port to a MultiMediaCard interface.

This design uses a Program Array Logic (PAL) device in the form of an ICT Inc., PEEL 22IV10AZ-25 CMOS Programmable Electrically Erasable Logic Device to convert an existing unidirectional SPI port to a bidirectional MultiMediaCard port.

### SPI2MMC PAL

The SPI2MMC PAL is intended to convert a host's two line, unidirectional (transmit and receive) port to a two line, directionally controlled, bidirectional port. The initial design was used to convert a host's SPI port to a MultiMediaCard port, but it could be used to convert any port with single unidirectional input and output ports to a MultiMediaCard single bidirectional DAT[0] / CMD port.

The SPI2MMC PAL is based on an ICT Inc., PEEL 22IV10AZ-25 CMOS Programmable Electrically Erasable Logic Device. The 22LV10AZ has a voltage operation range between +2.7V and +3.6V that exactly matches the effective operating range of the SanDisk MultiMediaCard. This device can be reviewed at ICT Inc.'s web site http://www.ictpld.com/products/22lv10az.htm.

The SPI2MMC PAL requires three outputs and one input from the host. There are two outputs to the MultiMediaCard. These signals are described in Table 1.

Signal Name	PAL Direction	Function	Corresponding Host SPI Line	PAL Pin Number
Тх	Input	Transmit line from the Host	MOSI	1
Td/Tc	Input	Transmit line Directional Control from the Host	-	2
Rx	Output	Receive line to the Host	MISO	21
Rd/Rc	Input	Receive line Directional Control from the Host		3
CMD	Input / Output	Corresponds to MultiMediaCard's CMD line		23
DAT	Input / Output	Corresponds to MultiMediaCard's DAT[0] line		22

Table 1 PAL Signal Definitions

### Signals

#### Тx

The Tx (or transmit) signal is the serial data output from the host. The PAL's Tx pin is a high impedance input.

#### Td/Tc

The Td/Tc signal is the directional control signal for the Tx line. Td/Tc is a digital output signal from the host. A "1" on the Td/Tc pin 2 applies the Tx pin 1's data to the DAT output pin 22. A "0" on the Td/Tc pin 2 applies the Tx pin 1's data to the CMD output pin 23. The PAL's Td/Tc pin is a high impedance input.

#### Rx

The Rx (or receive) signal is the serial data input to the host. The PAL's Rx pin is a digital output that "rests" at a logic "1" value when no data is being received. The Rx will always equal "1" when Tx is "0" and Td/Tc = Rd/Rc. This prevents "feedback" of the host's transmitted data to the receive line, so the user does not receive what he sends.

#### Rd/Rc

The Rd/Rc signal is the directional control signal for the Rx line. Rd/Rc is a digital output signal from the host. A "1" on the Rd/Rc pin 3 applies the DAT line's data input pin 22 to the Rx pin 21. A "0" on the Rd/Rc pin 3 applies the CMD line's data input pin 23 to the Rx pin 21. The PAL's Rd/Rc pin is a high impedance input.

#### CMD

The CMD (or command) signal is one of two bi-directional serial data ports connected directly to the MultiMediaCard. The PAL's CMD pin acts as both a digital input from the MultiMediaCard's CMD pin 2 and as an output from the host's Tx line. The PAL's CMD line always "rests" at a logical "1" so that either the Tx line or the MultiMediaCard's CMD line can drive pin 23.

#### DAT

The DAT (or data) signal is one of two bi-directional serial data ports connected directly to the MultiMediaCard. The PAL's DAT pin acts as both a digital input from the MultiMediaCard's DAT[0] pin 7 and as an output from the host's Tx line. The PAL's DAT line always "rests" at a logical "1" so that either the Tx line or the MultiMediaCard's DAT line can drive pin 22.

#### Limitations

The current implementation of the SPI2MMC PAL provides no MultiMediaCard clock signal. It assumes that a valid and "data aligned" clock is provided by the host.

Note that the PEEL 22IV10AZ-25 has a propagation delay of 25n seconds. Host system's using MultiMediaCard clock speeds approaching 20MHz may need to check for data misalignment due to this delay.

A limited number of PAL programmers can correctly program the PEEL 22lV10AZ-25 low voltage PAL. One such Programmer is System General's AllWriter Universal Programmer. System General Corporation's web site is http://www.sg.com.tw/HomePage.htm.

# UniDirectional to BiDirectional Serial Data Conversion for the MultiMediaCard



Figure 1 Schematic

UniDirectional to BiDirectional Serial Data Conversion for the MultiMediaCard



Figure 2 PAL Circuit Equivalent Schematic

## PAL ABEL File

module	e _SPI2MMC						
title	'2 wire Uni-	-direction to	o 2 wire Bi-d	lirecti	ional ser	rial in	iterface
Stephe	en R. Martin	Applicatio	ons Engineeri	ng, Sa	anDisk Co	orp.	
Sunnyv	vale CA 1 I	December 1998	3 '				
SPI2MN	MC device	e 'P22V1	LO';				
" Inpu	ıts						
	TX TD_TC RD_RC	pin 1; pin 2; pin 3;					
" Out <u>r</u>	puts						
	CMD DAT RX RXD	pin 23; pin 22; pin 21; pin 20;	" Interim Ra	signa	al (un-f:	iltered	1)
	X,C,L,H	= .X., .C.	., 0, 1;				
equati	ions						
	CMD = TX	<pre># TD_TC;</pre>					
	DAT = TX	# !TD_TC;					
	RXD = (CMD	& !(RD_RC))	# (DAT & (RI	D_RC));	;		
	RX = RXD & (I	# (!(TD_TC) RD_RC) & !RXI	& !TX & !(RI ));	D_RC) &	2 !RXD) =	# ((TD_	_TC) & !TX
"test_	_vectors						
п	([TX,	TD_TC,	RD_RC]	->	[CMD, I	DAT, F	2X])
II	[ 0,	Ο,	0]	->	[ 0,	1,	1 ];
п	[ 0,	0,	1]	->	[ 0,	1,	1 ];
"	[ 0,	1,	0]	->	[ 1,	Ο,	1 ];
II	[ 0,	1,	1]	->	[ 1,	Ο,	1 ];
п	[ 1,	0,	0]	->	[ 1,	1,	1 ];
II	[ 1,	0,	1]	->	[ 1,	1,	1 ];

### UniDirectional to BiDirectional Serial Data Conversion for the MultiMediaCard

II	[ 1,	1,	0]	->	[ 1,	1,	1 ];
II	[ 1,	1,	1]	->	[ 1,	1,	1 ];

end



